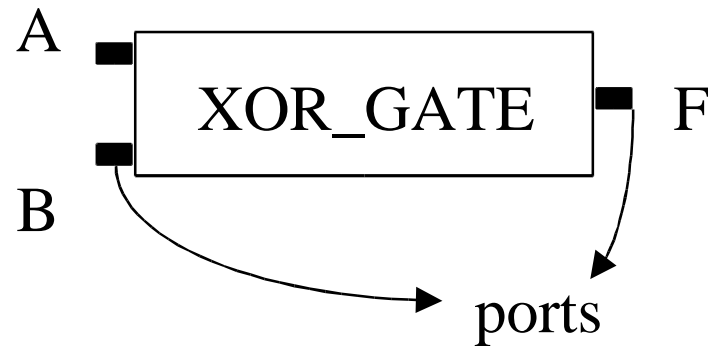


# Getting Started with Verilog

- ❑ Verilog is used to describe **hardware**, not software
- ❑ Verilog code is composed of a number of modules
- ❑ Modules are like functions or methods: they describe the interface of a component and its implementation
- ❑ Components modeled by a module can be primitive or complex objects
- ❑ Models can be implemented behaviorally or structurally

# A Verilog Module



```
module xor_gate (A, B, F);  
    input A, B;  
    output F;  
    assign F = (A & B) | (~A & ~B);  
endmodule
```

# Data Types

- Many data types in Verilog, but we will use a small subset:

```
integer i; // used for loop indicies
```

```
reg r1;  
reg [31:0]r2;
```

```
wire sigA, sigB;  
wire [31:0]sigC;  
tri busD;  
tri [31:0]busE;
```

# Literals

□ General form is `[size] ['radix]value`

`0`

`10`

`'b10`

`'h10`

`4'b100`

`4'bx`

`8'b0100_1001`

`8'o170`

# Declarations

```
module mymod (inbus, outbus);  
  
    parameter bus_width = 32;  
    parameter rise_delay = 20;  
  
    input [31:0] inbus;  
    output [31:0] outbus;  
  
    reg [31:0] regA;  
  
    wire somesig;  
  
endmodule
```

# Operators

## □ Logical

$A \&\&B$     $A || B$     $!A$     $\sim A$     $A \&B$     $A | B$     $A \sim ^\wedge B$

## □ Reduction

$\&A$     $\sim \&A$     $|A$     $\sim |A$     $^\wedge \sim A$     $\sim ^\wedge A$

## □ Relational

$A == B$     $A != B$     $A < B$     $A <= B$     $A > B$     $A >= B$     $A === B$     $A !== B$

## □ Shift

$A << B$     $A >> B$

## □ Arithmetic

$A + B$     $A - B$     $A * B$     $A / B$     $A \% B$

## □ Conditional, concatenate, replicate

$A ? B : C$     $\{A, B\}$     $\{A\{B\}\}$

# Continuous Signal Assignment

- ❑ Consists entirely of boolean equations
- ❑ References only wire signals
- ❑ Constantly re-evaluates whenever inputs change

```
assign f = (a & ~b) OR (~a & b);
```

# Structural Models

- ❑ Defines a module using components
- ❑ Defines internal signals to connect components
- ❑ All basic gates are available

```
wire s1, s2;  
  
nor(s1, s2, f);  
and(a, b, s1);  
nor(a, b, s2);
```

# Example Structural Model

```
module component1 (in1, in2, out);  
    input in1, in2;  
    output out;  
    assign out = (in1 & in2) | (~in1 & in2);  
endmodule
```

```
module mainmod (a, b, c, d, e);  
    input a, b, c, d;  
    output e;  
    wire w1, w2;  
    and(a, b, w1);  
    or(c, d, w2);  
    component1 inst1 (w1, w2, e);  
endmodule
```

# always Statements

## □ Behavioral models

```
always @( <sensitivity-list> )  
begin  
    <procedural-statments>  
    <if-else>  
    <case>  
    <while, for, repeat>  
end
```

# Sensitivity List

- ❑ Sensitivity list tells simulator when to evaluate the `always` block's code
- ❑ When any signal in the list changes its value, the `always` block is executed
- ❑ Special constructs `posedge` and `negedge` allow edge-triggered (flip-flop) models

# always Example

```
//  
// an 8-bit 2-to-1 mux  
//  
wire control;  
reg [7:0]a, [7:0]b, [7:0]c;  
  
always @(control or a or b)  
begin  
    if (control == 1)  
        c <= b;  
    else  
        c <= a;  
end
```

# Example using case statement

```
//  
// an 8-bit 4-to-1 mux  
//  
wire [1:0]control;  
reg [7:0]a, [7:0]b, [7:0]c, [7:0]d, [7:0]e;  
  
always @(control or a or b or c or d)  
begin  
    case (control)  
        0: e <= a;  
        1: e <= b;  
        2: e <= c;  
        3: e <= d;  
    endcase  
end
```

# initial Statements

## □ Simulation models - testbenches

```
initial
begin
    procedural-statments
    if-else
    case
    while, for, repeat
end
```

# Statements

- ❑ All statements end with a semi-colon ;
- ❑ Compound statements bracketed with  
begin ... end

```
begin
```

```
    a = b + c ;
```

```
    b = b & d ;
```

```
end
```

# Control Flow Statements

```
if (<condition>)
```

```
    <statement>
```

```
else
```

```
    <statement>
```

```
case (<expression>)
```

```
    <value> : <statement>
```

```
    <value> : <statement>
```

```
    default : <statement>
```

```
endcase
```

```
for (<initial>; <condition>; <increment>)
```

```
    <statement>
```

# Combinational Logic

- ❑ Use continuous assignments or ...
- ❑ always block with inputs in the sensitivity list

```
module some_logic (a, b, c, d, e);  
    input a, b, c, d;  
    output e;  
    reg s1;  
    assign e = s1 | d;  
    always @(a or b or c)  
        if (a & ~b)  
            s1 = c;  
        else  
            s1 = ~a;  
endmodule
```

# Assignment Statements

```
//continuous assignment
assign a = (b | c) & d;

always @(b or c or d)
begin
    //procedural blocking assignment
    a = (b | c) & d;

    //procedural non-blocking assignment
    a <= (b | c) & d;
end
```

# Non-Blocking Assignments

- ❑ Evaluate at the time of execution
- ❑ Complete (and update the variable) after all events at the current time
- ❑ Used only inside an `always`, and only to assign a `reg` or `integer`
- ❑ Only assign a given variable once
- ❑ Used in implementing sequential logic

# Sequential Circuits - Simple FF

- Use an always to control the inputs

```
module flip-flop (clk, d, q);  
    input clk, d;  
    output q;  
  
    always @(clk or d)  
        if (clk)  
            q <= d;  
  
endmodule
```

# Edge-Triggered FF

- Use `posedge` to control the **clock only**


```
module flip-flop (clk, d, q);  
    input clk, d;  
    output q;  
  
    always @(posedge clk)  
        q <= d;  
  
endmodule
```

# Asynchronous Reset or Preset


- ❑ Use posedge to control the **clock and reset**

```
module flip-flop (clk, rst, d, q);  
    input clk, rst, d;  
    output q;  
  
    always @(posedge clk or posedge rst)  
        if (rst == 1)  
            q <= 0;  
        else  
            q <= d;  
  
endmodule
```

# A Simple Example

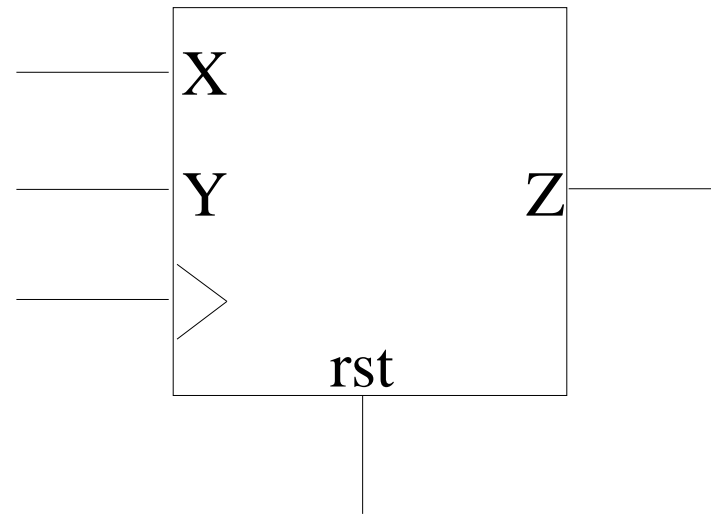

# Example Circuit

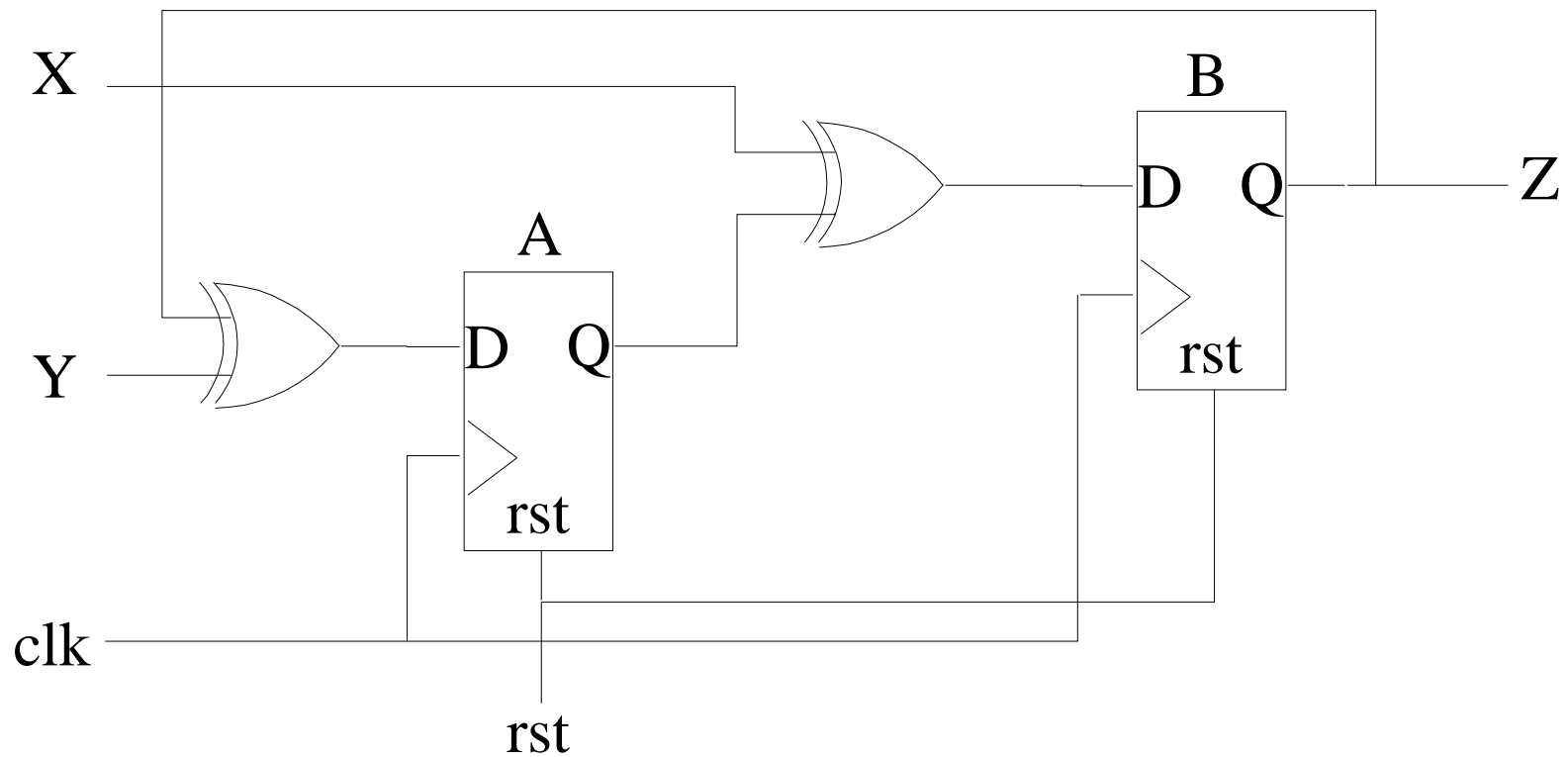

```
module example (clk, rst, x, y, z);
  input clk, rst, x, y;
  output z;
  wire da, db;
  reg qa, qb;
  assign da = y ^ qb;
  assign db = x ^ qa;
  assign z = qb;
  always @(posedge clk or posedge rst)
    if (rst == 1)
      qa <= 0;
    else
      qa <= da;
  always &(posedge clk or posedge rst)
    if (rst == 1)
      qb <= 0;
    else
      qb <= db;
endmodule
```

```
module example (clk, rst, x, y, z);
  input clk, rst, x, y;
  output z;
  reg qa, qb;
  assign z = qb;
  always @(posedge clk or posedge rst)
    if (rst == 1)
      qa <= 0;
    else
      qa <= y ^ qb;
  always &(posedge clk or posedge rst)
    if (rst == 1)
      qb <= 0;
    else
      qb <= x ^ qa;
endmodule
```

```
module example (clk, rst, x, y, z);
  input clk, rst, x, y;
  output z;
  reg qa, qb;
  assign z = qb;
  always @(posedge clk or posedge rst)
    if (rst == 1)
      begin
        qa <= 0;
        qb <= 0;
      end
    else
      begin
        qa <= y ^ qb;
        qb <= x ^ qa;
      end
endmodule
```

# Registers

- ❑ Registers are exactly like edge-triggered flip-flops but ...
  - ❑ They usually have more than one bit
  - ❑ They have more complex logic in the body

```
always @(posedge clk or negedge rst)
  if (rst == 0)
    register <= 0;
  else
    begin
      <register logic goes here>
    end
```

```

// data register
always @(posedge clk or negedge rst)
if (rst == 0)
    dregister <= 0;
else
    if (dload == 1)
        dregister <= dreg_in;

// shift register
always @(posedge clk or negedge rst)
if (rst == 0)
    sregister <= 0;
else
    case (scontrol)
        1 : sregister <= sregister >> 1;
        2 : sregister <= sregister << 1;
        3 : sregister <= sreg_in;
    endcase

```

```

// counter
always @(posedge clk or negedge rst)
if (rst == 0)
    counter <= 0;
else
    if (cload == 1)
        counter <= cnt_in;
    else if (count == 1)
        counter <= counter + 1;

// dreg with mux on input
always @(posedge clk or negedge rst)
if (rst == 0)
    dregister <= 0;
else
    case (mcontrol)
        0 : dregister <= abus;
        1 : dregister <= ~abus;
        2 : dregister <= abus & bbus;
        3 : dregister <= abux + bbus;
    endcase

```

# Testbenches

- ❑ Used to test a design
- ❑ Generates all external stimulus, including clock and reset
- ❑ Uses an initial block to sequence the test
- ❑ May use many language constructs NOT used in a hardware model

# Testbench Template

```
// no arguments here
module testbench;

    wire <declare a wire for each output>;
    reg <declare a reg for each input>;

    initial
    begin
        <test sequence goes here>
    end

    // this is a 20s clock
    always #10
        clk <= ~clk;

    // here we declar an instance of the design
    design uut (<input/output signals go here>)
endmodule
```

# Controlling Time in Verilog

- ❑ Several statements can cause a process to wait
  - ❑ To wait for a specific period of time
    - `#10; // waits for 10s`
    - `#param; // waits for the time specified by the parameter`
  - ❑ To wait for a specific event to occur
    - `@(<event-list>); // just like the always sensitivity list`

# Testbench Example

```
module testbench;
  reg clk, rst, x, y;
  wire z;
  always #10
    clk = ~clk;
  initial
  begin
    x = 0;
    y = 0;
    rst = 0;
    #5;
    rst = 1;
    #40;
    rst = 0;
    @(posedge clk);
    x = 1;
    @(posedge clk);
    x = 0;
  end
endmodule
```

# Testbench Example

```
y = 1;  
@(posedge clk);  
x = 1;  
@(posedge clk);  
@(posedge clk);  
y = 0;  
@(posedge clk);  
x = 0;  
@(posedge clk);  
@(posedge clk);  
y = 1;  
@(posedge clk);  
x = 1;  
@(posedge clk);  
x = 0;  
y = 0;  
@(posedge clk);  
end  
example uut (clk, rst, x, y, z);
```

```
endmodule
```


# Testbench Example2

```
module testbench;
    reg clk, rst, start;
    reg [31:0]multiplier;
    reg [31:0]multiplicand;
    wire [63:0]product;
    wire busy;
    initial
    begin
        clk = 0;
        rst = 0;
        start = 0;
        multiplier = 0;
        multiplicand = 0;
        #10;
        rst = 1;
        #40;
        rst = 0;
        $display("reset done");
        @(posedge clk);
        $display("starting multiply");
        multiplier = 8;
        multiplicand = 22;
        start = 1;
        @(posedge busy);
        $display("busy is high");
        start = 0;
        multiplier = 0;
        multiplicand = 0;
        @(negedge busy);
        $display("busy is low");
        $finish;
    end

    always #10
        clk = ~clk;

    multiplier uut (clk, rst, start, busy,
        multiplier, multiplicand, product);
```

# State Machines in Verilog

 

```

module moore_machine (clk, rst, x, z);
    input clk, rst, x;
    output z;
    reg [1:0]state, next_state;
    parameter [1:0] A=2'b00, B=2'b01, C=2'b11;

    assign z = (state == C); // Moore output


    always @(posedge clk or posedge rst)
        if (rst == 1)
            state <= A;
        else
            state <= next_state;

    always @(state, x)
        case (state)
            A: if (x == 1) next_state <= B else next_state <= A;
            B: if (x == 1) next_state <= A else next_state <= C;
            C: if (x == 1) next_state <= A else next_state <= B;
        endcase

endmodule

```

# State Machines in Verilog

 

```

module moore_machine (clk, rst, w, x, y, z);
    input clk, rst, w, x, y;
    output z;
    reg [1:0]state, next_state;
    parameter [1:0] A=2'b00, B=2'b01, C=2'b11;

    assign z = (state == C); // Moore output

    always @(posedge clk or posedge rst)
        if (rst == 1)
            state <= A;
        else
            state <= next_state;

    always @(state, w, x, y)
        case (state)
            A: if (x) next_state <= B else next_state <= A;
            B: if (x & y) next_state <= A else next_state <= C;
            C: if (W & x) next_state <= A else next_state <= B;
        endcase

endmodule

```

```

module moore_machine (clk, rst, w, x, y, z);
    input clk, rst, w, x, y;
    output z;
    reg [2:0]state, next_state;
    parameter [2:0] A=3'b001, B=3'b010, C=3'b100;

assign z = state[2]; // Moore output

always @(posedge clk or posedge rst)
    if (rst == 1)
        state <= A;
    else
        state <= next_state;

always @(state, w, x, y)
    case (state)
        A: if (x) next_state <= B else next_state <= A;
        B: if (x & y) next_state <= A else next_state <= C;
        C: if (W & x) next_state <= A else next_state <= B;
    endcase

endmodule

```